

Name \_\_\_\_\_

Date \_\_\_\_\_

## Circuitry Venn Diagram

Directions: Complete separate closed circuit. List characteristics, functions, and structures in each of the overlapping areas.

**Open Circuit**

**Closed Circuit**

