

Name _____

Date _____

Circuitry Venn Diagram

Directions: Complete separate closed circuit. List characteristics, functions, and structures in each of the overlapping areas.

Open Circuit

Closed Circuit

