

Name \_\_\_\_\_

Date \_\_\_\_\_

## Circuitry Venn Diagram

Directions: Complete separate open and closed circuit. List characteristics, differences, and similarities in your own words.

**Open Circuit**

**Closed Circuit**

