

Name _____

Date _____

Circuitry Venn Diagram

Directions: Complete separate open and closed circuit. List characteristics, differences, and similarities in your own words.

Open Circuit

Closed Circuit

