

Name _____

Date _____

Circuitry Venn Diagram

Directions: Compare open and closed circuits. List characteristics, similarities, and differences in your own words.

Open Circuit

Closed Circuit

