

Circuit symbols

Name: _____ Date: _____

LO: _____

Match the correct symbol with the word:




Bulb



Buzzer



Switch

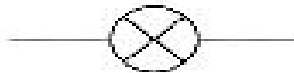

Motor





Cell (Battery)



Wire



 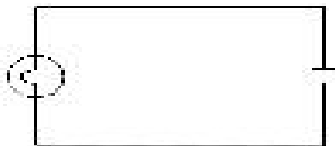Here is a drawing of a simple circuit with 1 bulb and 1 cell:



1) Redraw, in the box provided, the same circuit BUT include a switch.