

d. Wire

6) State true or false for the following statements.

- a. Filament in the bulb produces electric current.
- b. Batteries are also called dry cells.
- c. Each dry cell has 2 terminals which must be connected to produce energy.
- d. We can use plastic or metals paper clips in a circuit tester.
- e. The more batteries connected in series, the brighter the bulbs.
- f. There are chemicals in dry cells that can react to produce energy

7) Identical components are used for the following circuits.

