


	$R_1$	$R_2$	$R_3$	Total	
<b>E</b>					Volts
<b>I</b>					Amps
<b>R</b>					Ohms
<b>P</b>					Watts


  
*Ohm's Law*    *Ohm's Law*    *Ohm's Law*    *Ohm's Law*