


| | R_1 | R_2 | R_3 | Total | |
|----------|-------|-------|-------|-------|-------|
| E | | | | | Volts |
| I | | | | | Amps |
| R | | | | | Ohms |
| P | | | | | Watts |



Ohm's Law *Ohm's Law* *Ohm's Law* *Ohm's Law*