


	R_1	R_2	R_3	Total	
E					Volts
I					Amps
R					Ohms
P					Watts



Ohm's Law *Ohm's Law* *Ohm's Law* *Ohm's Law*