

### Changing circuits

Name: .....

Look at each circuit diagram below. If you think the bulb or bulbs will light, put a tick in the box. If you do not think the bulb or bulbs will light, put a cross in the box.

	
	
	