

# Circuits



Name: \_\_\_\_\_ Date: \_\_\_\_\_

Draw a circuit diagram that will cause the bulb to glow. Label the circuit as a series circuit, a parallel circuit, or a combination circuit.

