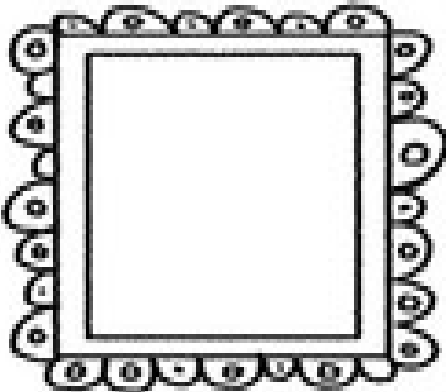


Name _____

Date _____


Electric Circuit Foldable: Series and Parallel Circuits

Series Circuit



Draw a picture of a series circuit.

Parallel Circuit

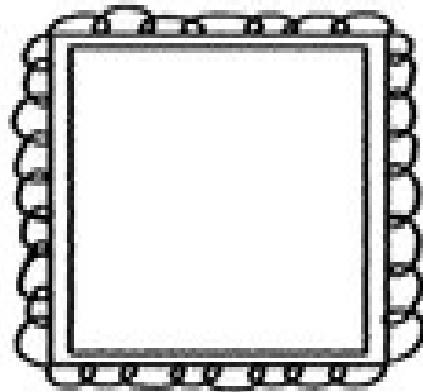

Draw a picture of a parallel circuit.

Match the boxes below to the correct vocabulary word.

This is a circuit that allows an electric current to flow along more than one path.	This is a circuit that allows only one path for the flow of electricity.
This type of circuit will not work if one or more light bulbs go out.	This type of circuit will work if one or more light bulbs go out.