

Find the current in the $2 + j 2$ ohm impedance the network of Fig. 11.9(a) using Norton's theorem.

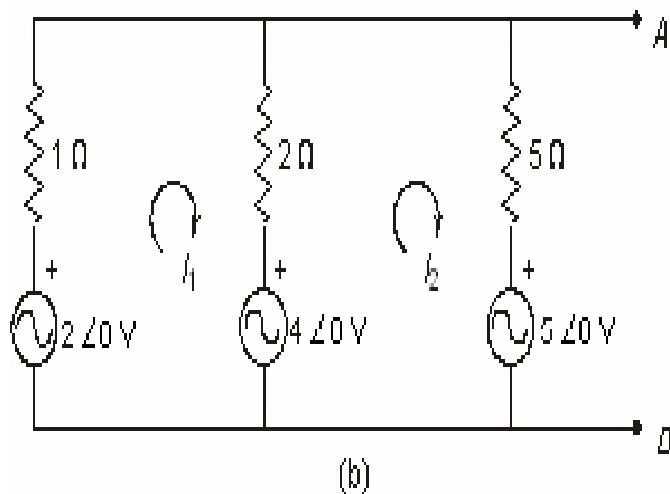
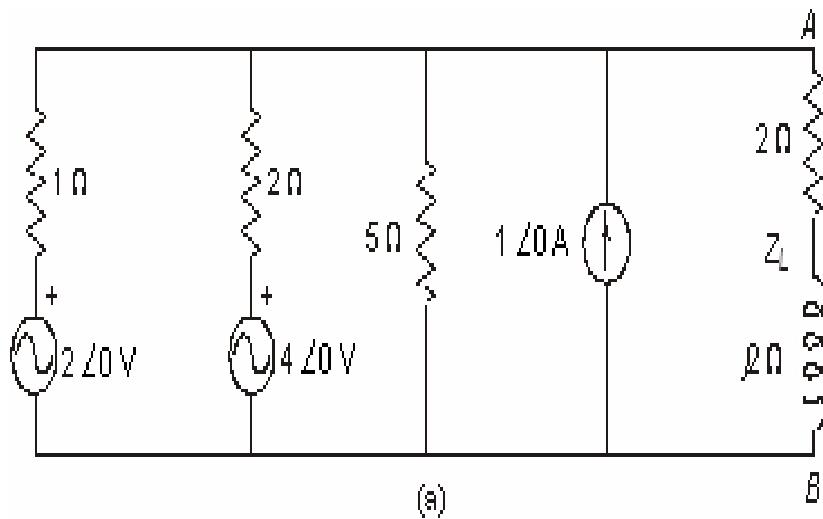


Fig. 11.9