



**Science investigation**

⚠ **Take extra care - ask an adult to supervise you.**  
Build a circuit using a battery, bulb, and alligator clip

Materials: Note design your own switch. You might  
use: paper, wood, metal tacks, and heavy-duty wire  
⚡ **Test** your switch.

On Off On Off On Off On Off

© 2013 Pearson Education, Inc. All rights reserved.