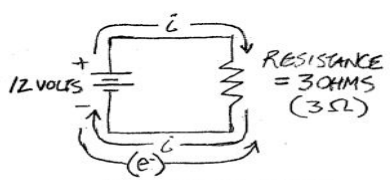


CR2


Q: IF YOU DOUBLE THE BATTERY VOLTAGE IN THE CIRCUIT BELOW
WHAT EFFECT WILL THIS HAVE ON THE CURRENT?
WHAT IF YOU DOUBLE THE RESISTANCE INSTEAD?

HW4-7
AGENDA
HOMEMADE
DISHWASHER
CURRENT
RESISTANCE
OHM'S LAW



1 COULOMB OF CHARGE
1 AMP (1 COULOMB/SEC)
BATTERY
VOLTAGE
WIRE

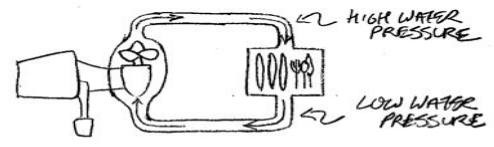RESISTANCE IMPEDES
CURRENT FLOW
RELEASING ENERGY



(LIKE DISHES IMPEDE
WATER FLOW)

RESISTANCE DEPENDS ON...

- LENGTH OF WIRE - LONGER => MORE RESISTANCE
- THICKNESS OF WIRE - THIN => MORE RESISTANCE (LIKE PINCHING A HOSE)
- WHAT WIRE IS MADE OF - GOLD => LOW RESISTANCE TUNGSTEN => HIGH RESISTANCE

(AQ) DOUBLING VOLTAGE => DOUBLES CURRENT
DOUBLING RESISTANCE => CUTS CURRENT IN HALF

GEORGE OHM'S LAW (1789-1854):

$$(\text{ELECTRIC POTENTIAL}) = (\text{CURRENT})(\text{RESISTANCE}) \quad V = iR \quad 1 \text{ VOLT} = (1 \text{ AMP})(1 \text{ OHM})$$

$$R = \frac{V}{i} \quad 1 \text{ OHM} (1 \Omega) \equiv \frac{1 \text{ VOLT}}{1 \text{ AMP}}$$

$$i = \frac{V}{R} \quad 1 \text{ AMP} = \frac{1 \text{ VOLT}}{1 \text{ OHM}}$$

(EX) HOW MUCH CURRENT IS FLOWING THROUGH THE BATTERY IN THE (AQ)?

$$V = iR \quad i = \frac{V}{R} = \frac{(12 \text{ VOLTS})}{(3 \Omega)} \left(\frac{(1 \text{ AMP})(1 \Omega)}{1 \text{ VOLT}} \right) = \boxed{4 \text{ AMPS}}$$

IF THE RESISTOR IS REPLACED WITH A LIGHTBULB AND THE CURRENT BECOMES 250 mA (MILLIAMPS) WHAT IS THE LIGHTBULB'S RESISTANCE?

$$V = iR \quad R = \frac{V}{i} = \frac{12 \text{ VOLTS}}{250 \text{ mA}} \left(\frac{(1 \text{ AMP})(1 \Omega)}{1 \text{ VOLT}} \right) = \boxed{48 \Omega}$$