



*NOTE: voltage sources  $vi_1$ ,  $vi_2$ ,  $vi_3$ , and  $vi_4$  are "dummy" sources set at zero volts each.*