

Name: \_\_\_\_\_

Use the Venn Diagram to compare and contrast series and parallel circuits.

