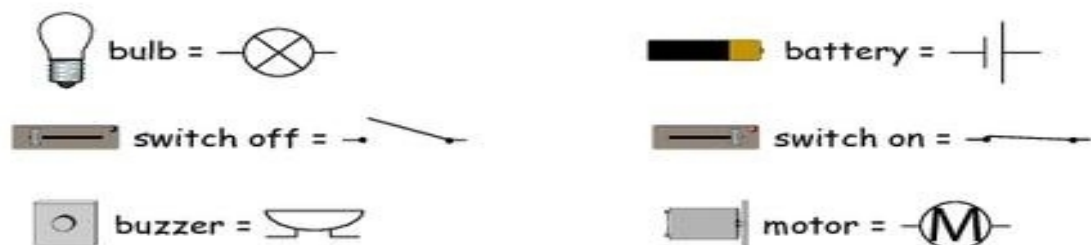


Name: \_\_\_\_\_ Subject: Year 4 Science  
 Date: \_\_\_\_\_ Unit: 4f Circuits and conductors

### Circuits

When drawing circuits we should use symbols for each part of the circuits, this makes it easier to draw and understand.

Look at the symbols below:



Draw the correct symbols below:

Buzzer	Bulb	Motor
Switch on	Battery	Switch off