

Name \_\_\_\_\_

Date \_\_\_\_\_

## Circuit's Venn Diagram

Directions: Compare series and parallel circuits. List characteristics, definitions, and draw pictures under the appropriate circle.

### Series Circuit

### Parallel Circuit

