

Ohm's Law worksheet

Name _____ Per: _____

1. The rate of electron flow is measured in (a) amperes (b) volts (c) ohms.
2. Potential difference is measurement of _____ and is symbolized in the ohms law equation as the letter (____) and the unit symbol (____). The rate of electron flow is called _____ and is measured in amps (A). The symbol for the flow of electrons in an equation is (____). The _____ (R) is measured in ohms (____).
3. Voltage = _____ times _____.
4. According to Ohm's Law, what effect will decreasing the resistance have on the current?
5. In a circuit, voltage and current are (a) directly proportional, (b) inversely proportional, (c) not proportional.
6. Rearrange Ohm's Law to answer the following; Current equals _____ divided by _____.
7. If the power source is set at 6V and R is 2 ohms, the current = _____
8. V=5volts, R= 10 ohms, I= _____.
9. If the voltage stays the same and the resistance is $\frac{1}{4}$ of its original, what will happen to the current?
10. If the current in the circuit is 7 amps and the resistance is 2 ohms the voltage = _____.
11. R= 30 ohms, I= 3A, V= _____
12. Resistance = _____ divided by _____.
13. If the power source is 12 V and the flow of electrons is 3A, what is the resistance?
14. V= 6V, I= 18A, R= _____

Extension Questions:

15. A _____ is the electric pressure required to produce one ampere of current in a circuit having one _____ of resistance.
16. One amp is one _____ per second. A coulomb is _____ electrons.

Ohm's Law worksheet

Name _____ Per: _____

1. The rate of electron flow is measured in (a) amperes (b) volts (c) ohms.
2. Potential difference is measurement of _____ and is symbolized in the ohms law equation as the letter (____) and the unit symbol (____). The rate of electron flow is called _____ and is measured in amps (A). The symbol for the flow of electrons in an equation is (____). The _____ (R) is measured in ohms (____).
3. Voltage = _____ times _____.
4. According to Ohm's Law, what effect will decreasing the resistance have on the current?
5. In a circuit, voltage and current are (a) directly proportional, (b) inversely proportional, (c) not proportional.
6. Rearrange Ohm's Law to answer the following; Current equals _____ divided by _____.
7. If the power source is set at 6V and R is 2 ohms, the current = _____
8. V=5volts, R= 10 ohms, I= _____.
9. If the voltage stays the same and the resistance is $\frac{1}{4}$ of its original, what will happen to the current?
10. If the current in the circuit is 7 amps and the resistance is 2 ohms the voltage = _____.
11. R= 30 ohms, I= 3A, V= _____
12. Resistance = _____ divided by _____.
13. If the power source is 12 V and the flow of electrons is 3A, what is the resistance?
14. V= 6V, I= 18A, R= _____

Extension Questions:

15. A _____ is the electric pressure required to produce one ampere of current in a circuit having one _____ of resistance.
16. One amp is one _____ per second. A coulomb is _____ electrons.