

Circuits



Name _____

Date _____

Write in the space above each circuit whether the bulb or bulbs would be
a) off b) glowing dimly c) glowing normally d) glowing brightly

