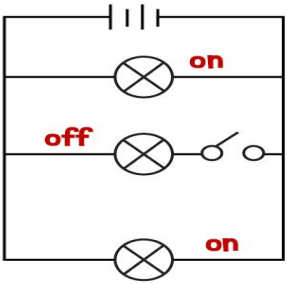
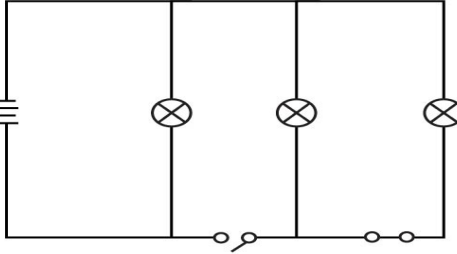
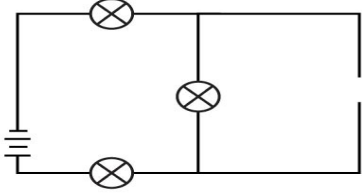
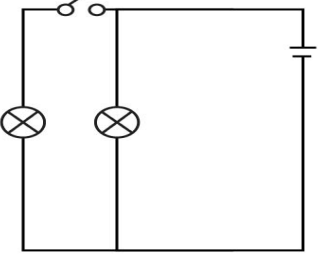
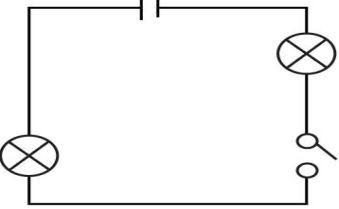


Name: _____ Date: _____

SERIES AND PARALLEL CIRCUITS

Determine if the bulb is glowing or not
by writing "on" or "off" next to the bulb.

	<p>1.</p> 
<p>2.</p> 	<p>3.</p> 
<p>4.</p> 	<p>5.</p> 