Name:	Date:

## SERIES AND PARALLEL CIRCUITS

Observe each circuit and label it as series or parallel.











