

R/Yr 1

NAME: \_\_\_\_\_


# Kaleidoscopes

reflection                      colour                      light waves                      reflective surfaces

Tick the shape you can see when you look down the tube.



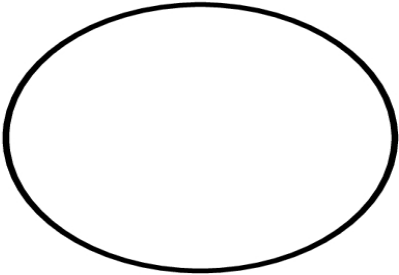Draw the pattern you can see when you look down the kaleidoscope.



# Circuits

circuit                      batteries                      chemical energy                      light energy

Circle whether the light was **ON** or **OFF** in the circuits that you make.

- |    |                 |       |                 |
|----|-----------------|-------|-----------------|
| 1) | Basic circuit   | Light | <b>ON / OFF</b> |
| 2) | One battery     | Light | <b>ON / OFF</b> |
| 3) | Change of order | Light | <b>ON / OFF</b> |