

## Circuit symbols

Name: \_\_\_\_\_ Date: \_\_\_\_\_

LO: \_\_\_\_\_

Match the correct symbol with the word:




**Bulb**



**Buzzer**



**Switch**

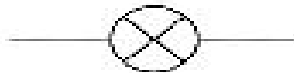

**Motor**





**Cell (Battery)**



 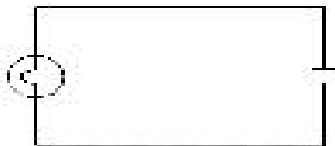**Wire**



Here is a drawing of a simple circuit with 1 bulb and 1 cell:



1) Redraw, in the box provided, the same circuit BUT include a switch.