





On the right circuit

Observations

To light up a bulb with a battery, you need to make a circuit. All the parts of a circuit must be connected in the right order for the bulb to light up. This is called making a complete circuit.

Science activity

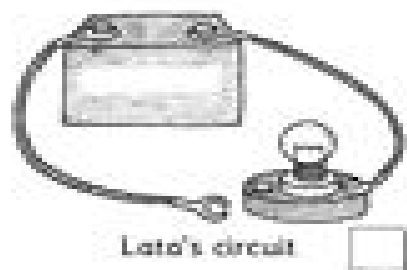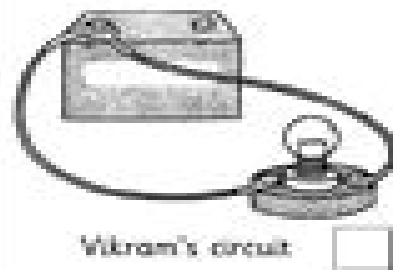Vikram, Allison, Morgan, and Lata each tried to make a bulb light up using a battery and wires. Who made the bulb light up? Place a check mark (✓) in the right box.



Science exploration

⚠ Take extra care - ask an adult to supervise you.

Ask an adult to help you set up a complete circuit.

