

Make the circuit work

Circuit Diagram



What are the components in this circuit?

Will electricity flow through this circuit?

Yes No

What is missing from this circuit to make it work?

Draw a diagram to complete the circuit that will allow the electricity to flow.

