

Name _____

Date _____

OPEN AND CLOSED CIRCUITS

Observe each diagram and label the circuit as open or closed!












