

5. A _____ is used to find out whether a material is a conductor of electricity.

Write True or False

1. Batteries cannot store electricity. ()
2. When the circuit is open, an electromagnet loses its magnetism. ()
3. The brightness of a bulb depends on its voltage. ()
4. Electricity can flow through an open circuit. ()
5. Electrical energy can be converted into heat energy. ()