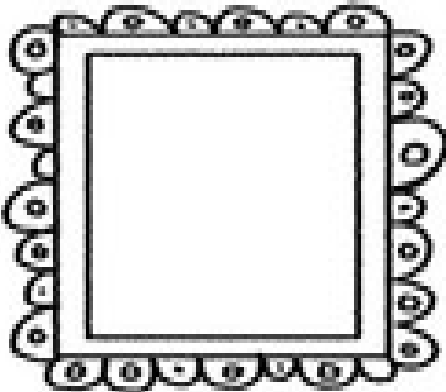


Name \_\_\_\_\_

Date \_\_\_\_\_


## Electric Circuit Foldable: Series and Parallel Circuits

### Series Circuit



Draw a picture of a series circuit.

### Parallel Circuit

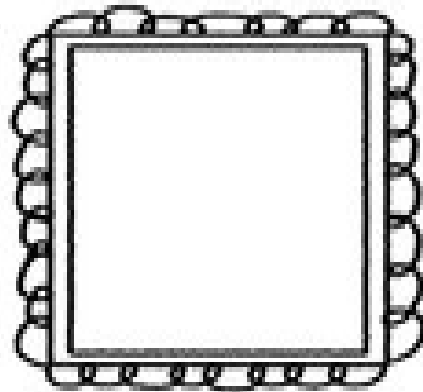

Draw a picture of a parallel circuit.

Match the boxes below to the correct vocabulary word.

This is a circuit that allows an electric current to flow along more than one path.	This is a circuit that allows only one path for the flow of electricity.
This type of circuit <b>will not work</b> if one or more light bulbs go out.	This type of circuit <b>will work</b> if one or more light bulbs go out.