

Competency: **Relay start/stop motor control circuit**    Version:

**Description**

Build a start/stop motor control circuit using an electro-mechanical relay and two (momentary) pushbutton switches

**Schematic**

**Parameters**

Motor latches in the energized state  
when "Start" switch is pressed and released

☐

Motor latches in the de-energized state  
when "Stop" switch is pressed and released

☐