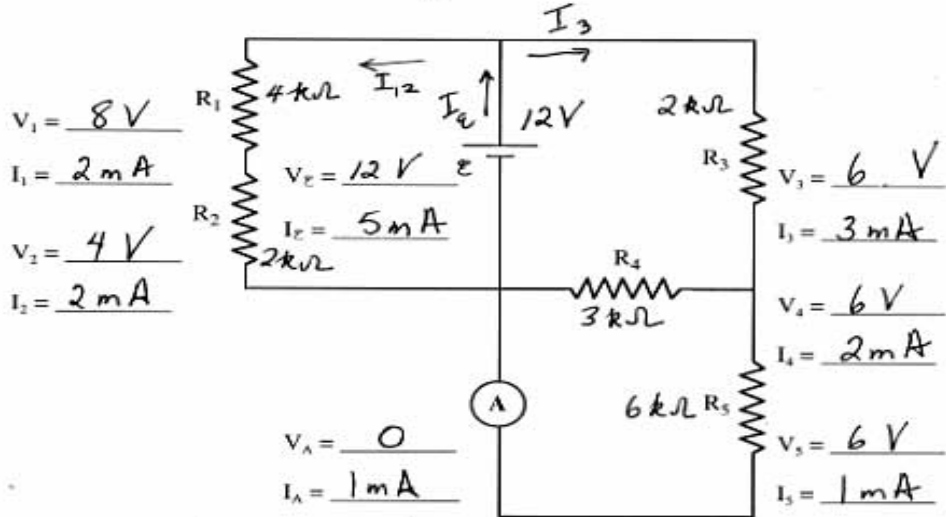


Answers:

$$I_e = I_{12} + I_3 = 2\text{mA} + 3\text{mA} = 5\text{mA}$$



①  $R_1$  &  $R_2$  in series (same current)

$$R_{12} = R_1 + R_2 = 6\text{k}\Omega$$

$$I_1 = I_2 = I_{12} = \frac{V_{12}}{R_{12}} = \frac{12\text{V}}{6\text{k}\Omega} = 2\text{mA}$$

$$V_1 = I_1 R_1 = 2\text{mA}(4\text{k}\Omega) = 8\text{V}$$

$$V_1 + V_2 = \mathcal{E} \rightarrow V_2 = 12 - 8\text{V} = 4\text{V}$$

② ideal ammeter has  $R_A = 0$

$$\text{so } V_A = I_A R_A = 0$$

and  $I_A = I_5 =$

④  $\text{A}$

③  $R_4 \parallel R_5$

$$\rightarrow R_{45} = \frac{1}{\frac{1}{R_4} + \frac{1}{R_5}} = \frac{1}{\frac{1}{3} + \frac{1}{6}}$$

$$= \frac{1}{\frac{1}{2}} = 2\text{k}\Omega$$

$R_{45}$  series w/  $R_3$

$$R_{345} = R_3 + R_{45} = 2\text{k}\Omega + 2\text{k}\Omega = 4\text{k}\Omega$$

$$I_3 = I_{45} = I_{345} = \frac{V_{345}}{R_{345}} = \frac{12\text{V}}{4\text{k}\Omega} = 3\text{mA}$$

$$V_3 = I_3 R_3 = 3\text{mA}(2\text{k}\Omega) = 6\text{V}$$

$$V_4 = V_5 = V_{45} = \mathcal{E} - V_3 = 12 - 6 = 6\text{V}$$

$$I_4 = \frac{V_4}{R_4} = \frac{6\text{V}}{3\text{k}\Omega} = 2\text{mA}$$

$$I_5 = I_3 - I_4 = 3 - 2\text{mA} = 1\text{mA}$$