

Name _____

Date _____

OPEN & CLOSED CIRCUIT

Observe each diagram and give "O" for open circuit and "C" for closed circuit.

