

Name \_\_\_\_\_

Date \_\_\_\_\_

# PARTS OF ELECTRICAL CIRCUIT

Look at the parts of electrical circuit below and write the name of each part.

battery  
wire

lamp  
voltmeter

ammeter  
switch

