

Name _____

Date _____

ELECTRICAL CIRCUIT

Tell whether the light bulb or bulbs will light or will not light based on the circuit.

will light

