

Name _____

Date _____

ELECTRIC CIRCUIT

Mark the circuit diagrams with a tick if you think the bulb will light. Put a cross if you think the bulb will not light.

