

Name _____

Date _____

SERIES AND PARALLEL CIRCUIT

Observe each circuit and give "S" for series circuit and "P" for parallel circuit.

