

Name _____

Date _____

SIMPLE CIRCUIT

Observe each electrical circuit below and identify which lamp is turning on by write "on" next to each lamp.

