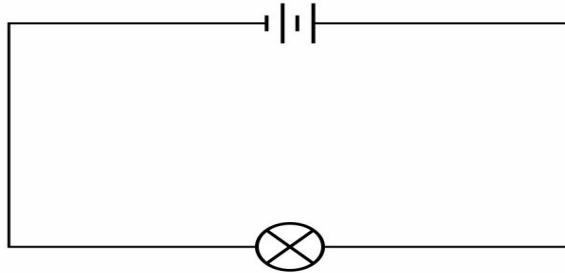


Name _____

Date _____

BUILDING ELECTRICAL CIRCUIT

Answer the questions below.




Is the circuit above complete? _____

Does the bulb work? _____

Why is it not practical? _____

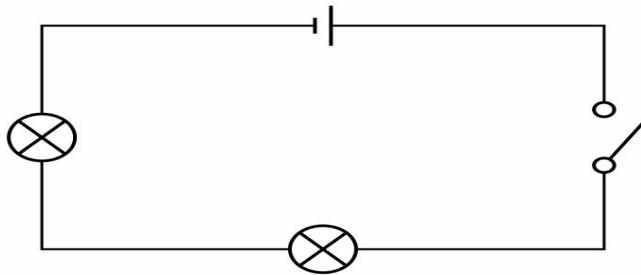How many cells are there in the battery? _____



How many wires did you use for this circuit? _____

Is the circuit complete when the switch is open? _____

What happens to the bulb when the switch is closed? _____

What needs to happen for the bulb to work? _____