

Circuits



Name _____ Date _____

Draw a circuit that will cause the bulbs to glow. Label the circuit as a series circuit, a parallel circuit, or a combination circuit.

