

Name _____ Date _____

SCIENCE EXERCISE

Fill in the correct term for each labeled part of the image below.

movie	positive	cells	switch	alarm clock
damage	gap	light	flows	put
socket	open	circuit	negative	wet

1. When the switch in a circuit is _____, there is a gap in the circuit.
2. Nina can turns the table lamp on or off by using a _____.
3. A _____ provides a path for electricity to flow.
5. The electric iron uses electricity from the mains when we plug it into _____.
10. There are two poles in battery, they are _____ and _____.
11. When the switch is closed, there is no _____ in the circuit.
12. Electricity _____ through the circuit, so the bulb light up.
9. Flashlight uses electricity from batteries to give off _____.
6. Mobile phone uses electricity from batteries or _____.
7. Fires caused by electricity can _____ the things.
8. The electric fan and toy car use electricity to _____.
14. Do not _____ your finger into the socket.
4. The sound from the _____ buzzer is so loud.
13. Electricity is dangerous for us when we touch it using _____ hands.