

Schematic**Given conditions**

$$V_{\text{signal}} =$$

$f_{\text{signal}} =$ Set by instructor without student's knowledge

Parameters

Measured
with oscilloscope

t_{period}

Measured
with counter

f_{signal}

Measured
with oscilloscope