



**FUNCTION GENERATOR**

Hz

1 10 100 1k 10k 100k 1M

square sine  $\square$   $\nabla$   $\nabla$  DC output

**FUNCTION GENERATOR**

Hz

1 10 100 1k 10k 100k 1M

square sine  $\square$   $\nabla$   $\nabla$  DC output

**FUNCTION GENERATOR**

Hz

1 10 100 1k 10k 100k 1M

square sine  $\square$   $\nabla$   $\nabla$  DC output

**OSCILLOSCOPE**

vertical  Y

Y/div  DC GND AC

trigger

timebase  X

X/div  DC GND AC